

## Table of Contents

<b>Basic Electricity .....</b>	<b>2</b>
Definitions .....	2
Relationships .....	2
Passive Sign Convention .....	2
Circuit Elements .....	2
Independent .....	2
Dependent .....	2
Resistors .....	2
Capacitors .....	2
Inductors .....	3
Op Amps .....	3
Voltmeter .....	3
Ammeters .....	3
<b>Analysis Methods .....</b>	<b>3</b>
KCL .....	3
KVL .....	3
Node-Voltage .....	3
Super-Nodes .....	3
Current Mesh .....	3
SuperMesh .....	4
Thévenin Equivalent .....	4
Norton Equivalent .....	4
Source Transform .....	4
Inductors and Capacitors .....	4
Sinusoidal Steady State .....	4
<b>AC .....</b>	<b>4</b>
Impedance and Reactance Equations .....	4
Sinusoidal Functions .....	4
<b>Power .....</b>	<b>5</b>

## Basic Electricity

### Definitions

**Voltage** is energy per unit charge.  $= \frac{dw}{dq} \left( \frac{J}{C} = V \right)$

**Current** is rate of charge flow.  $= \frac{dq}{dt} \left( \frac{C}{s} = A \right)$

**Power** is energy per unit time.  $= \frac{dw}{dt} \left( W = VA = \frac{J}{s} \right)$

**Resistance** is the capacity to impede flow of current.  $= R \ (\Omega)$

**Nodes** are points where two or more elements join

**Loops** are any closed path in circuit

**Meshes** are loops not containing other loops

### Relationships

$$p = vi = i^2 R = \frac{v^2}{R}$$

$$v = iR$$

### Passive Sign Convention

Passive Element(Load) = Power Dissipated  $> 0$

Active Element = Power Dissipated  $< 0$

### Circuit Elements

#### Independent

**Ideal Voltage Sources** deliver a prescribed voltage independent of current flow.

**Idea Current Sources** deliver a prescribed current independent of voltage

#### Dependent

**Voltage/Current Control Voltage/Current Sources** depend on Independent Elements.

**VCVS.**  $= v_s = \alpha v_x$

**CCVS.**  $= v_s = \beta i_x$

**VCCS.**  $= i_s = \gamma v_x$

**CCCS.**  $= i_s = \gamma i_x$

### Resistors

**Resistors** impede the flow of charge. **Ohm's Law** states  $v = iR$ . **Shorts** are when voltage across is 0. Ex:  $R = 0 \rightarrow V = i(0) = 0$ . **Opens** are when current is 0. Ex:  $R = \infty \rightarrow i = \frac{v}{\infty} = 0$ .

**Series:**  $R_{eq} = R_1 + R_2 + \dots + R_n = \sum_n R_n$ ,  $V_n = \frac{R_n}{R_{eq}} V_s \rightarrow V_1 = \frac{R_1}{R_1 + R_2} V_s$

**Parallel:**  $G_{eq} = G_1 + G_2 + \dots + G_n = \sum_n G_n$ ,  $i_n = \frac{\frac{1}{R_n}}{\frac{1}{R_{eq}}} i_s = \frac{G_n}{G_{eq}} i_s \rightarrow i_1 = \frac{R_2}{R_1 + R_2} i_s$ ,  $R_{eq} =$

$$\sum_n 1/R_n \rightarrow R_{eq\ TWO} = \frac{R_1 R_2}{R_1 + R_2}$$

### Capacitors

**Capacitors** store energy and are model as an open in DC steady state. Series add in parallel and parallel add in series.

$$q = cv, i = c \frac{dv}{dt} \rightarrow i = c(0) = 0, v = \frac{1}{c} \int_{t_0}^t i dt + v(t_0), w_c = \frac{1}{2} cv^2$$

### Inductors

**Inductors** store energy and are model as closed in DC steady state. Series add in series and parallel add in parallel.

$$v = L \frac{di}{dt} \rightarrow v = L(0) = 0, i = \frac{1}{L} \int_{t_0}^t v dt + i(t_0), w_L = \frac{1}{2} Li^2$$

### Op Amps

**Op Amps** can add, subtract, multiply or divide input voltage signals.

$$v_p = v_n, R_{in} \rightarrow \infty, R_{out} = 0, A = \frac{V_o}{V_s} = \frac{V_o}{V_p - V_n} \rightarrow A \rightarrow \infty, -V_{cc} \leq V_o \leq V_{cc}$$

Procedure to solve for  $v_o$

- 1) Solve for  $v_p$  or  $v_n$  (whichever is not connected to  $v_o$ ).
- 2) Use Node-Voltage Method for the one connected to  $v_o$ .
- 3) Substitute Equation from step (1) and (2) and solve.

### Voltmeter

**Voltmeters** find voltages & are connected in parallel.

$$R_{estiance \text{ into circuit}} = \frac{v_{fullscale}}{y} \rightarrow \text{Ideally } \infty, R_v = \frac{v_r}{y}, v_R = fullscale - x$$

### Ammeters

**Ammeters** find currents & are connected in series.

$$R_{estiance \text{ into circuit}} = \frac{x}{i_{fullscale}} \rightarrow \text{Ideally } 0, R_a = \frac{x}{i_r}, i_R = fullscale - y$$

## Analysis Methods

### KCL

**Kirchhoff's current law** states charge is conserved.  $\sum_{node} i = 0$

### KVL

**Kirchhoff's voltage law** states energy is conserved.  $\sum_{loop} v = 0$

### Node-Voltage

- 1) Define a Reference Node to 0V
- 2) Label all independent nodes (voltage unknown)
- 3) Define current directions
- 4) Write current in terms of Node-Voltage ( $i = \frac{V_A - v_B}{R}$ ) and substitute into KCL equations
- 5) Solve
- 6) Use Node-Voltage to find anything else in the circuit.

### Super-Nodes

**Super-Nodes** are 2 non-reference nodes connected directly by a voltage source. To solve apply KVL in Loop with Super.

### Current Mesh

- 1) Define current loop directions.
- 2) Express voltage in terms of Current Meshes ( $v = i_1 R_1$ ) and substitute into KVL equations.
- 3) Solve
- 4) Use Mesh to find anything else in circuit

### SuperMesh

To solve **SuperMeshes** find a closed path that does include the current source and apply KCL.

### Thévenin Equivalent

A **Thévenin equivalent circuit** is a simple circuit with a voltage source and resistor in series.

- 1) Set all independent source to 0 (Short VS and open CS).
- 2)  $R_{th} = R_{eq}$
- 3)  $v_{th} = v_{OC}$  (Set load to open).

### Norton Equivalent

A **Norton equivalent circuit** is a simple circuit with a current source and resistor in parallel.

- 1)  $R_N = R_{th}$
- 2)  $i_N = i_{sc}$  (Set load to closed).

### Source Transform

A Thévenin equivalent circuit can be transformed into a Norton equivalent circuit and vice versa.  $v_{th} = i_N R$  in Series is equal to  $i_N = \frac{v_{th}}{R}$  in Parallel. The resistor remains constant and the sources change following Ohm's Law.

### Inductors and Capacitors

- 1) Find time constant.  $\tau = Rc = \frac{L}{R}$
- 2) Capacitors:  $v_{0-} = v_{0+}$ , Inductors:  $i_{0-} = i_{0+}$
- 3) Find  $X_f$  as  $t \rightarrow \infty$
- 4) Standard form:  $x(t) = x_f + (x_0 - x_f)e^{-\frac{t}{\tau}}$

### Sinusoidal Steady State

- 1) Find  $\omega$
- 2) Convert from time domain to frequency domain
  - a. Sinusoidal voltages and currents to phasors
  - b. R, L, C to Impedance
- 3) Solve linear system  $v = Zi$
- 4) Convert back to time domain

## AC

### Impedance and Reactance Equations

	Impedance	Reactance
Resistor	$R$	0
Inductor	$j\omega L$	$\omega L$
Capacitor	$-\frac{j}{\omega C}$	$-\frac{1}{\omega C}$

### Sinusoidal Functions

$$v(t) = v_m \cos(\omega t + \phi) = v_m \angle \phi, T = \frac{2\pi}{\omega}, \omega = 2\pi f$$

## Power

**Maximum Power:**  $Z_L = Z_{th} \rightarrow p_{L\max} = \frac{v_{th}^2}{4R_{th}} (DC)$ ;  $Z_L = Z_{th}^* \rightarrow P_{L\max} = \frac{|v_{th(RMS)}|^2}{4R_L} (AC)$

**Apparent ( $S$ ), Average( $P$ ), and Reactive( $Q$ ) Power:**  $S = P + jQ = v_{RMS} i_{RMS}^*$

**Power/Reactive Factor:**  $pf = \cos(\theta_v - \theta_i)$ ,  $rf = \sin(\theta_v - \theta_i)$ ;

**Average Power:**  $P = \frac{1}{2} v_m i_m \cos(\theta_v - \theta_i) = v_{RMS} i_{RMS} \cos(\theta_v - \theta_i)$

**Reactive Power:**  $Q = \frac{1}{2} v_m i_m \sin(\theta_v - \theta_i) = v_{RMS} i_{RMS} \sin(\theta_v - \theta_i)$

**Units:**  $P \rightarrow \text{watts}$ ,  $q \rightarrow \text{VAR}$ ,  $S \rightarrow \text{VA}$