

Table of Contents

RLC Circuits	2
Properties and Definitions.....	2
Analysis Methods	2
Equivalent RLC.....	2

RLC Circuits

Properties and Definitions

2nd Order Circuits because they are represented by 2nd order differential equations

Natural Response is the response of the circuit without a power supply.

Step Response is the response of the power supply on the circuit.

Resonant Radian Frequency is dependent on equivalent inductors and capacitors ($\omega_o = \sqrt{\frac{1}{LC}}$)

Neper Frequency measures the rate at which the transient response diminishes ($\frac{1}{2RC}$ or $\frac{R}{2L}$) - PS

Overdamped is when the Neper Frequency is greater than the Resonant Rad. Freq. ($\alpha^2 > \omega_o^2$)

- Standard form: $x(t) = x_f + A_1 e^{-s_1 t} + A_2 e^{-s_2 t}$
- $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2}$

Underdamped is when the Neper Frequency is less than the Resonant Rad. Freq. ($\alpha^2 < \omega_o^2$)

- Standard form: $x(t) = x_f + (A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t))e^{-\alpha t}$
- $\omega_d = \sqrt{\omega_o^2 - \alpha^2}$

Critically damped is when the Neper Frequency is equal to Resonant Rad. Freq. ($\alpha^2 = \omega_o^2$)

- Standard form: $x(t) = x_f + A_1 t e^{-\alpha t} + A_2 e^{-\alpha t}$

Analysis Methods

Equivalent RLC

- 1) Find Neper and Resonant Rad. Frequencies. $\alpha = \frac{1}{2RC}$ or $\frac{R}{2L}$ (par. ser.); $\omega_o = \sqrt{\frac{1}{LC}}$
- 1) Capacitors: $v_{0-} = v_{0+}$, Inductors: $i_{0-} = i_{0+}$
- 2) Find X_f as $t \rightarrow \infty$
- 3) Compare Neper and Resonant Rad. Frequencies to find out response
 - a. $\alpha^2 > \omega_o^2$
 - i. Standard form: $x(t) = x_f + A_1 e^{-s_1 t} + A_2 e^{-s_2 t}$
 - ii. $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_o^2}$
 - b. $\alpha^2 < \omega_o^2$
 - i. Standard form: $x(t) = x_f + (A_1 \cos(\omega_d t) + A_2 \sin(\omega_d t))e^{-\alpha t}$
 - ii. $\omega_d = \sqrt{\omega_o^2 - \alpha^2}$
 - c. $\alpha^2 = \omega_o^2$
 - i. Standard form: $x(t) = x_f + A_1 t e^{-\alpha t} + A_2 e^{-\alpha t}$
- 4) Calculate the coefficient giving known parameters (A_1 & A_2)

S-Domain Transforms

- 1) Find Initial conditions if capacitor or inductor is present.
 - a. $v_c(0-) = v_c(0+)$ and $i_L(0-) = i_L(0+)$
- 2) Transform circuit to find impedance and transformed sourced values.
 - a. Resistors don't change impedance ($Z_R = R$), Sources are divided by S.
 - b. Capacitor impedances are inversely related to capacitance and are divided by S
 - i. $Z_C = \frac{1}{sC}$

ii. Capacitor Series Voltage Source

$$1. V_c = \frac{v_c(0)}{s}$$

iii. Capacitors Reverse Parallel Current Source

$$1. I_c = C v_c(0)$$

c. Inductor impedances are directly related to inductance and are multiplied by S.

$$i. Z_L = LS$$

3)

i. Inductors

ii.

iii. If an I.C. for a capacitor is zero

b. , ignore element source in transform.

4) Transform Circuit

a. If I.C. equal zero, drop the source in the transform

5) Solve

6) Partial Fraction

7) Inverse Laplace